

CE 241 Final Exam Review
(90 minutes)
(Open-Book, Open-Note)

① Number System Conversions

Binary \rightarrow Decimal \rightarrow Octal \rightarrow HEX \rightarrow Arbitrary

② Addition, subtraction, Multiplication, Division in Binary

③ Boolean Algebra and the theorems.

$$A + BC = (A + B)(A + C) \quad \bar{A}B + A\bar{B} = \bar{A}\bar{B} \oplus AB$$

④ K Map, sop, pos, static hazard, timing Diagram (time delay)


⑤ FA, HA, MUX, Decoder (lecture 17)

⑥ SR latch, SR FF, JK FF, JK master slave FF, TFF, DFF,

⑦ Counter, shift register (lecture 22), switch debouncing
(NOR, NAND)

⑧ Mealy / Moore state machine

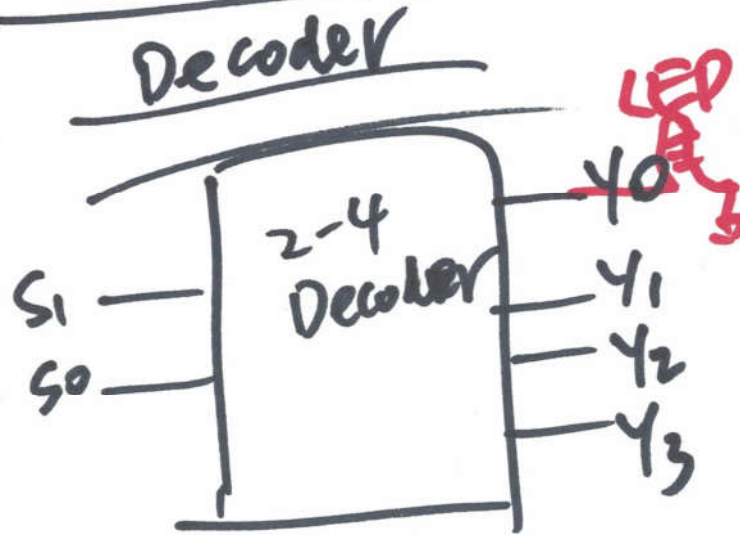State Program \rightleftharpoons Sequential Circuit



S ₁	S ₀	Y ₀	Y ₁	Y ₂	Y ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

No. of patterns = Possible No. Input Combination

3 patterns = 2 bits

6 patterns = 3 bits

9 patterns = 4 bits




7 Segment Display

$\begin{matrix} f \\ a \end{matrix} \begin{matrix} g \\ b \end{matrix} \begin{matrix} e \\ c \\ d \end{matrix}$

2 0 3 4 5 6 7


0-7 : 8 different outputs

S_2	S_1	S_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	0	0
0	0	1	0	0	1	1	0	1	1
0	1	0	0	1	0	1	1	1	1
0	1	1	0	0	0	1	1	0	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	0	1	1	0	1	1
1	1	0	1	1	1	1	0	1	1
1	1	1	1	1	1	1	1	1	1

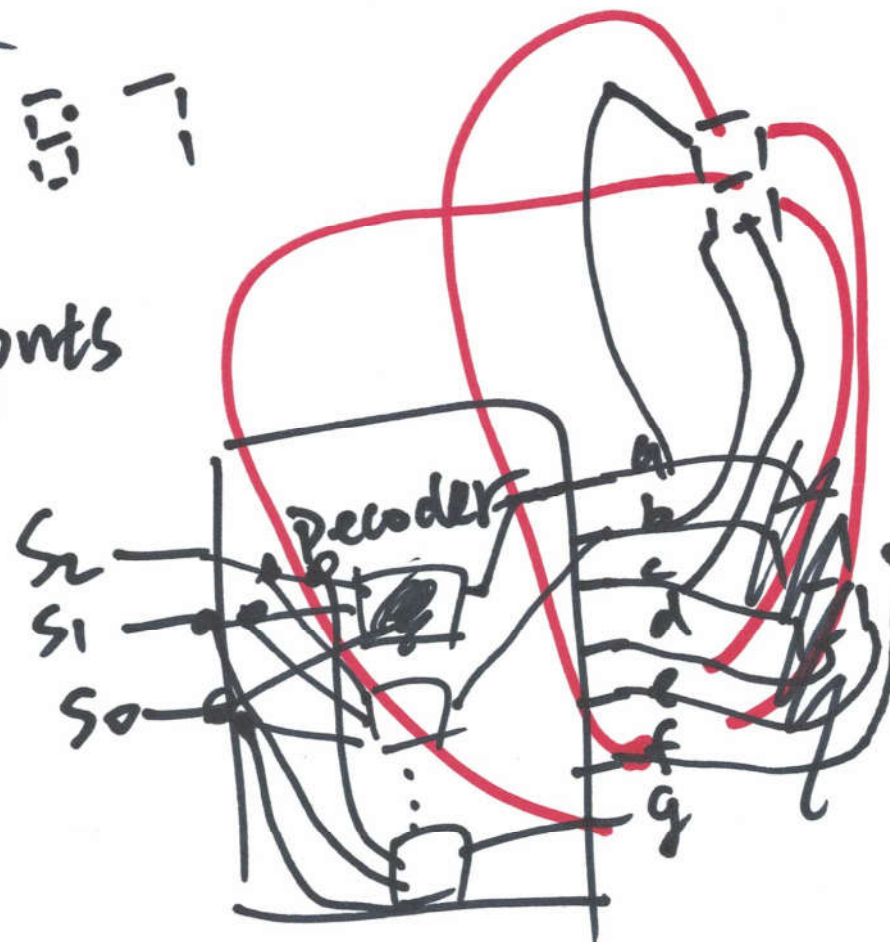

$s_2 \backslash s_1 s_0$	00	01	11	10
0	1	0	①	0
1	1	1	0	1
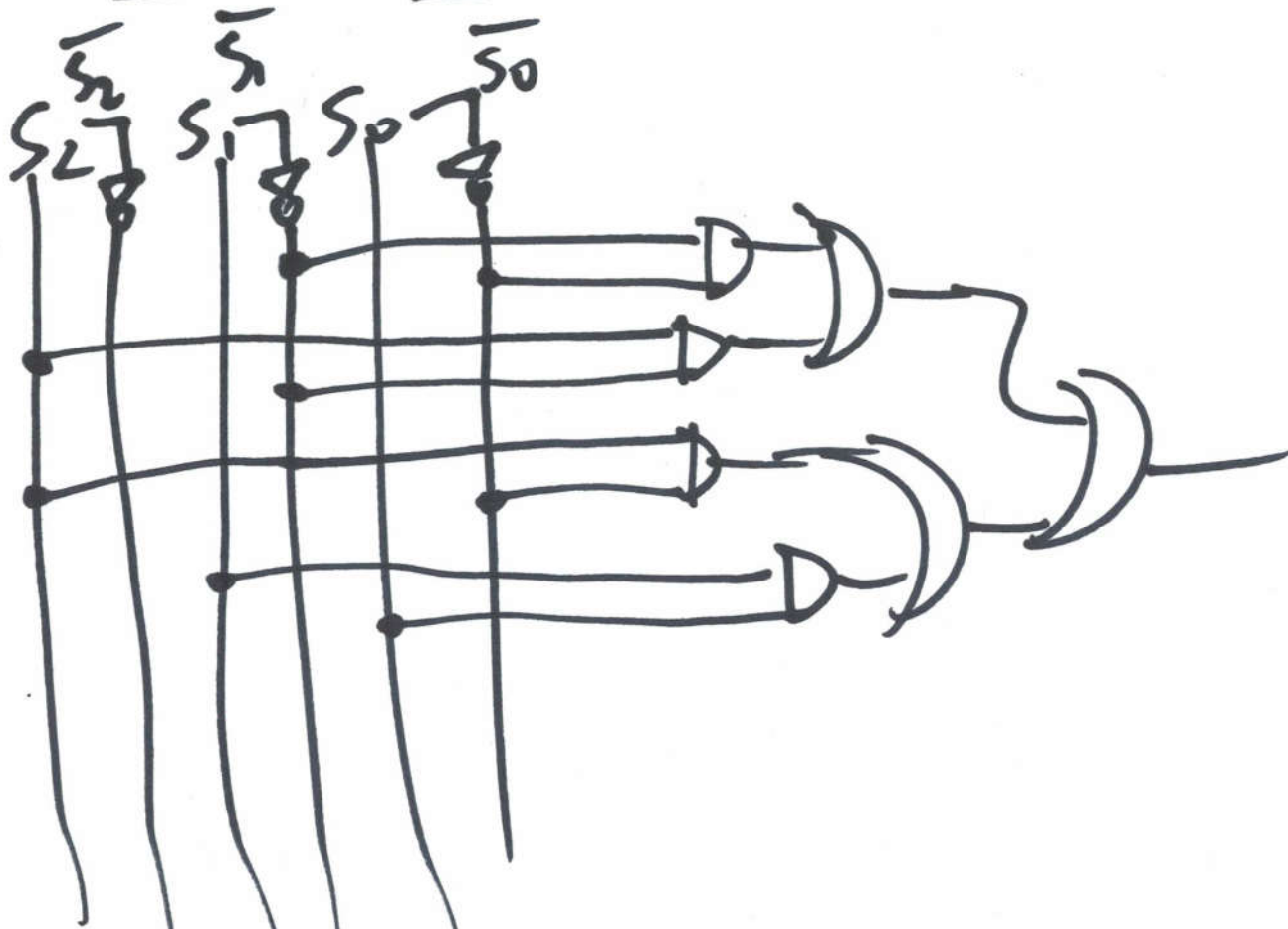
$$a = \overline{s_1} \overline{s_0} + s_2 \overline{s_1} + s_2 \overline{s_0} + s_1 s_0$$



④

5-7
3 numbers

S_1	S_0	a	b	c	d	e	f	g
0	0	1	0	1	1	0	1	1
0	1	1	1	1	0	1	1	1
1	0	0	0	0	1	1	1	0

$$a = \bar{S}_1 \bar{S}_0 + \bar{S}_1 S_0 = \bar{S}_1 (\bar{S}_0 + S_0) = \bar{S}_1$$



5