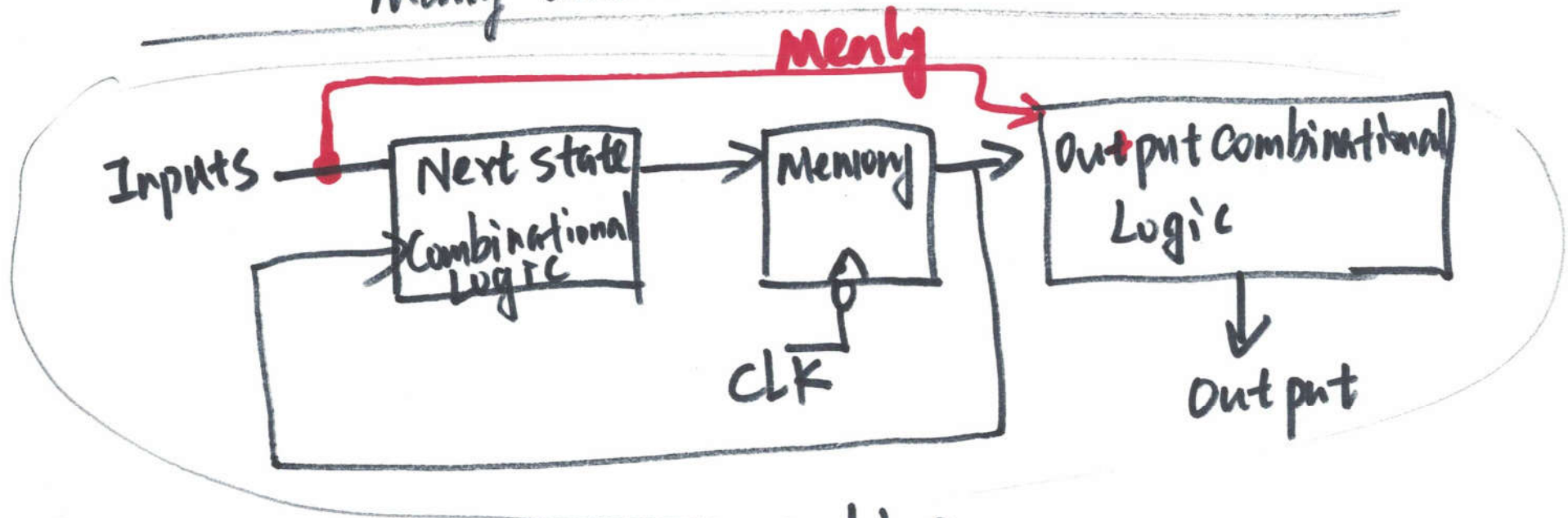


Mealy and Moore State Machines



Moore State Machine

△ Mealy State machine: The output is the function of present state as well as the input.

△ Moore State machine: The output is the function of the present state only.

A very Simple Example:


JKFF

$Q' = Q + 1$

J	K	Q	Q'
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(mem)
(mem)


(Toggle)

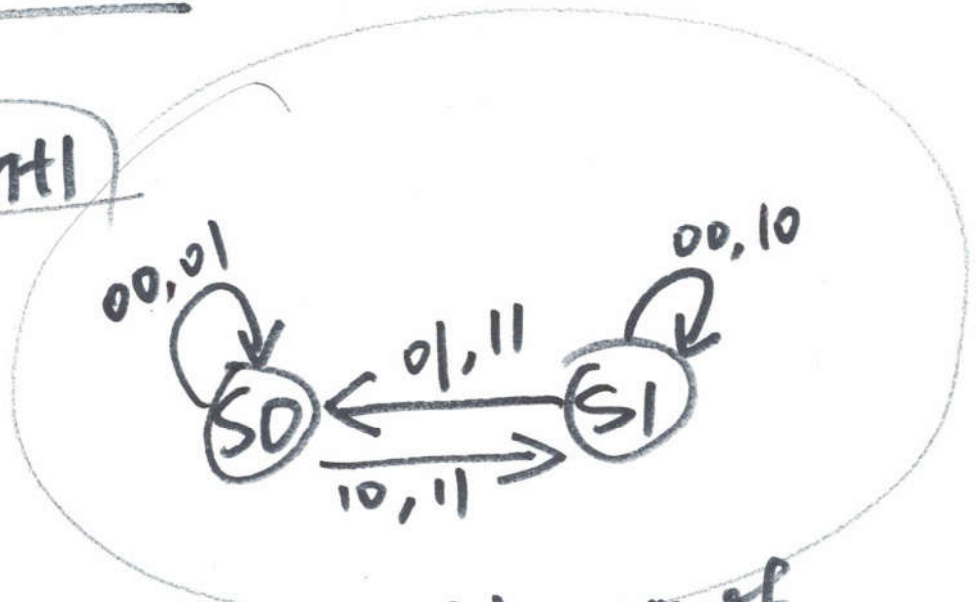

State Diagram of
the JK FF.

Examples: Moore machines

△ Circuit → Diagram

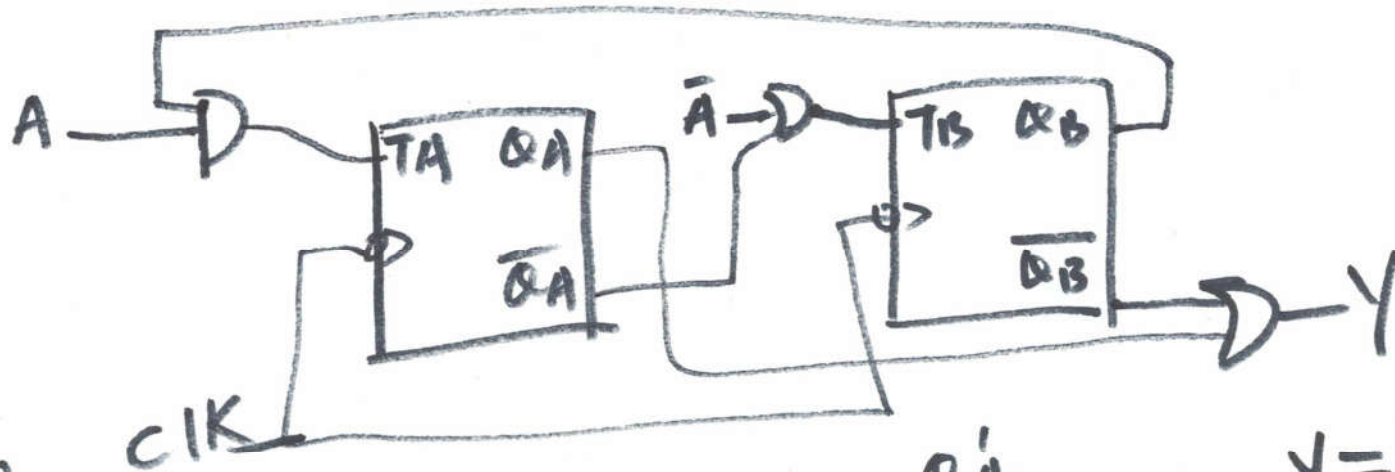

Step 1:

A	Q _A	Q _B	Q _A '	Q _B '	T _A	T _B	Y	Y'
0	0	0	0	1	0	1	0	0
0	0	1	0	0	0	1	0	1
0	1	0	1	0	0	1	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	1	0	1	0	1
1	0	1	0	0	1	1	0	1
1	1	0	0	1	0	0	1	1
1	1	1	0	0	1	0	1	0

Q_A':

T _A	Q _A '
0	Q _A
1	Q _A '

Q_B':

T _B	Q _B '
0	Q _B
1	Q _B '

$$T_A = A \cdot Q_B$$


$$T_B = \bar{A} + \bar{Q}_A$$


$$Y = \bar{Q}_B + Q_A$$

$$Y' = \bar{Q}_B' + Q_A'$$

QAB

Y

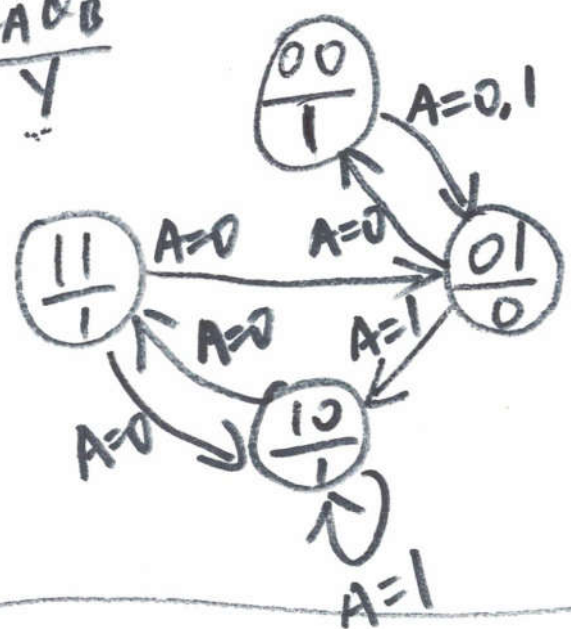

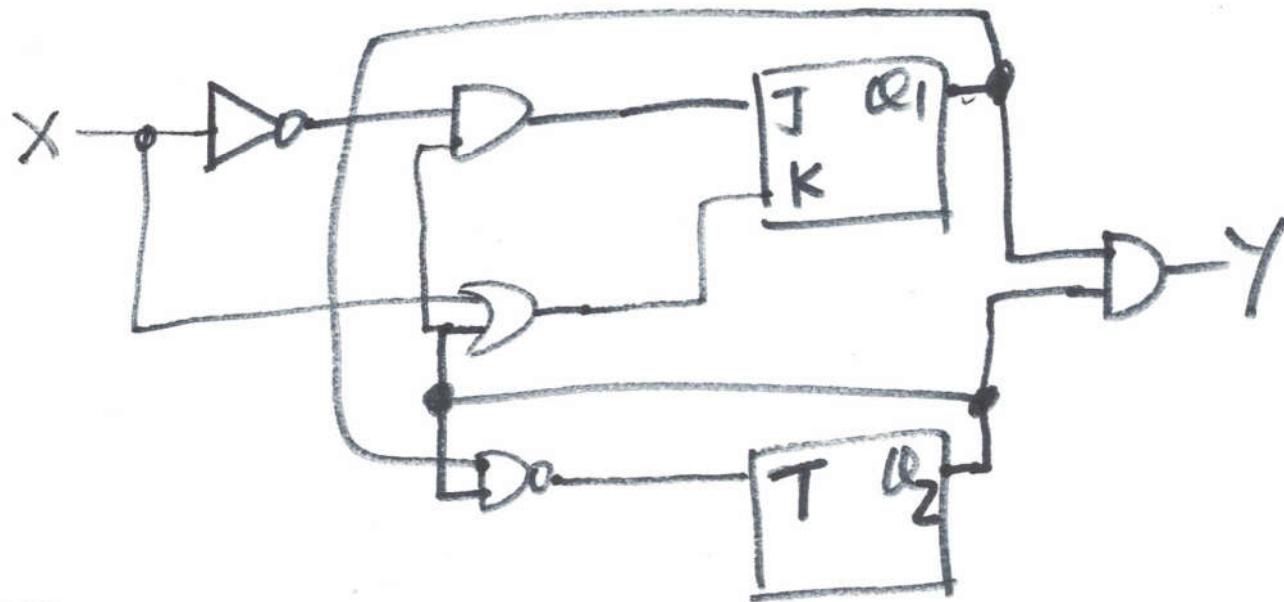

Step 1:

X	Q_1	Q_2	Q_1'	Q_2'	J	K	T	Y'
0	0	0	0	1	0	0	1	0
0	0	1	1	0	0	1	1	0
0	1	0	1	1	0	0	1	0
0	1	1	0	0	1	1	0	0
1	0	0	0	1	0	1	1	0
1	0	1	0	0	0	1	1	0
1	1	0	0	1	0	1	1	0
1	1	1	0	0	1	0	1	0

$$J = \bar{X} \cdot Q_2$$

$$K = X + Q_2$$

$$T = \overline{Q_1 \cdot Q_2}$$

Q_1' :

J	K	Q_1'
0	0	0
0	1	0
1	0	1
1	1	1

$$Y = Q_1 \cdot Q_2$$

$$Y' = Q_1' \cdot Q_2'$$

Q_2' :

J	K	Q_2'
0	0	0
0	1	0
1	0	1
1	1	1

$$\frac{0.02}{4}$$

